



fritzing

Here is a modified circuit with a buzzer added in.

Can you write the code so that:

- 1) the LED is on if the button is not pressed
- 2) when the button is pressed, the LED turns off and the buzzer makes a noise

HINT

Start with the code we used for the button

How can we code the buzzer so that it makes a different sound?

HINT

Think about how we changed the brightness of an LED